

# CONTINUOUS INTERNAL EVALUATION - 2

Dept: FY

Sem / Div: I D/E/F

Sub: Basic Electronics

S Code: 18ELN14

Date: 06/3/2021

Time: 9:30-11:00 am

Max Marks: 50


Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
----	-----------	-------	-----	------

## PART A

1 a	Explain the operation of enhancement type of MOSFET with a neat circuit diagram.	6	L2	CO2
b	Explain op-amp as integrator with a neat circuit diagram.	7	L2	CO3
c	Explain different input modes of an op-amp.	6	L2	CO3
d	The transistor in CE configuration with $R_c=1k\Omega$ , $\beta_{dc}=125$ . Determine 1. $V_{ce}$ at $V_{in}=0V$ 2. $I_b(\min)$ to saturate the collector current. 3. $R_b(\max)$ when $V_{in}=8V$ . $V_{ce}(\text{sat})$ can be neglected.	6	L2	CO1

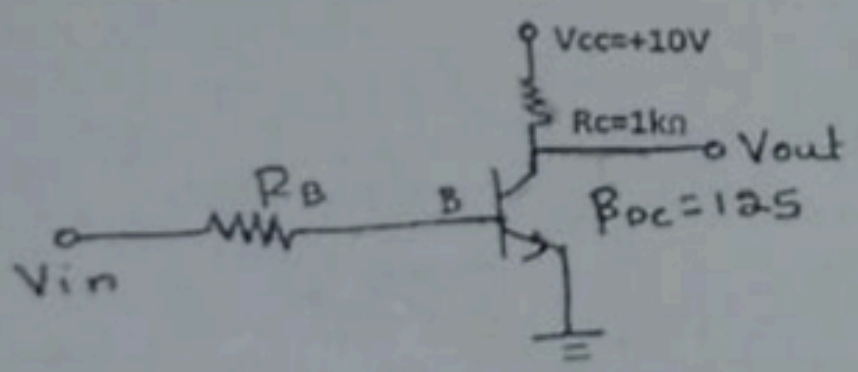

OR

2 a	Explain CMOS as inverter with a neat circuit diagram With its advantages.	8	L2	CO2
b	Explain the following terms with respect to op-amp. 1. CMRR 2. Slew rate 3. Input bias current 4. PSRR	8	L2	CO



c	Explain the drain and transfer characteristics of a n-channel JFET with neat circuit diagram.	8	L2	CO1
d	Show that the ripple factor of a half-wave rectifier is 1.21 and efficiency is 40.5%	5	L3	CO1

### PART B

3 a	Explain with neat circuit diagram and waveform, the working of <u>center-tap</u> full wave rectifier. Show that efficiency of full-wave rectifier is 81%.	8	L2	CO1
b	A Zener diode has a breakdown voltage of 10V. It is supplied from a voltage source varying between 20-40V in series with a resistance of 820Ω. Using an ideal Zener model, obtain the minimum and maximum Zener currents.	6	L3	CO1
c	Explain the functional block diagram of 78XX series voltage regulator.	6	L2	CO1
d	For a n-channel JFET if $I_{DSS} = 9 \text{ mA}$ $V_P = -6 \text{ V}$ . Calculate $I_D$ at $V_{GS} = -4 \text{ V}$ and $V_{GS}$ at $I_D = 3 \text{ mA}$ .	5	L3	CO2

### OR

4 a	Explain how zener diode helps in voltage regulation with neat circuit diagram	8	L2	CO1
b	A full wave rectifier uses 2 diodes having internal resistance of 20Ω each. The transformer rms secondary voltage from center to each end is 50V. Find $I_m$ , $I_{dc}$ , $I_{rms}$ , and $V_{dc}$ if the load is 980Ω.	6	L3	CO1
c	Explain the operation of half-wave rectifier with capacitor filter with neat circuit diagram and waveform.	6	L2	CO1
d	For a JFET $I_{DSS} = 9 \text{ mA}$ and $V_{GS(off)} = -8 \text{ V}$ . Determine drain current for $V_{GS} = -4 \text{ V}$ and $V_{GS} = -6 \text{ V}$	5	L3	CO2

Naveena C  
21/01/21

Prepared by: Naveena C

g. kant  
HOD 29/01/21